

## 109-2 Digital System Design Homework 1

0. After logging into the workstation, you should source two files to ensure that you can use nc-verilog and nWave successfully.

```
source /usr/cad/cadence/cshrc
source /usr/spring_soft/CIC/verdi.cshrc
```

### 1. 8-bit Carry Ripple Adder (40%)

In problem 1, you need to model an 8-bit carry ripple adder (CRA). The input and output ports are illustrated in Figure 1. This is similar to the lab in *Switching Circuit and Logic Design* course.

 


Figure 1

#### (1) (20%)

Modify “adder\_gate.v” which contains the module name and input/output ports. Design at **gate level**. We suggest you design a *full adder* first and then instantiate eight full adders in the higher hierarchy. Use the given test bench, “adder\_gate\_test.v” to verify your design. To simulate, use the following command:

```
ncverilog adder_gate_test.v adder_gate.v +access+r
```

A waveform file “adder.fsdb” will be dumped. You can use waveform viewer to help your debugging:

```
nWave &
```

When the window appears, you need to open the dumped fsdb file and then add signals to the waveform viewer. Show your waveform result in the report.

(2) (10%)

Use continuous assignment (use “**assign**”) to describe the transfer between input signals and output signals of an 8-bit carry ripple adder. You can use arithmetic operators. Start with the “adder.v” file, which contains the module name and input/output ports. To simulate, use the following command:

```
ncverilog adder_test.v adder.v +access+r
```

(3) (10%)

The **critical path** of a combinational circuit is defined as follows: on every path from input to output, the longest (largest sum of delay) one is the critical path. Specify 1ns delay for each Verilog primitive in (1) (*and*, *or*, ...). Illustrate the critical path of your design in the report and calculate the sum of the delay. Try to modify the 2<sup>nd</sup> line in “adder\_gate\_test.v”. Use different cycle time and report the correctness.

```
`define CYCLE 20.0
```

Verify the timing of your design with waveform viewer.

```
ncverilog adder_gate_test.v adder_gate.v +access+r
```

## 2. 8-bit Barrel-shifter (40%)

Barrel-shifter has a simple and regular structure and is usually used in different microprocessors. Problem 2 asks you to design an 8-bit logical shift-left barrel-shifter (shift to MSB with zero padding from LSB).

Figure 2 shows an operating example of barrel shifter. The control input (shl4, shl2, and shl1) determines the amount of shifting. The “shl4” performs a shift-left by 4 bits, the “shl2” performs a shift-left by 2 bits, and the “shl1” performs a shift-left by 1 bit. Thus, the 8-bit barrel shifter in Figure 2 shifts the input data left by 5 bits. The output data are left-shifted input data and 5 zeros.

 


Figure 2

Figure 3 shows the regular structure of barrel shifter (shift from MSB to LSB). For an 8-bit barrel shifter, there are three levels of multiplexers. Each level contains eight 2-to-1 multiplexers. To efficiently describe the structure, we suggest you partition the design into three levels: *mux*, *level*, and a *barrel shifter*.

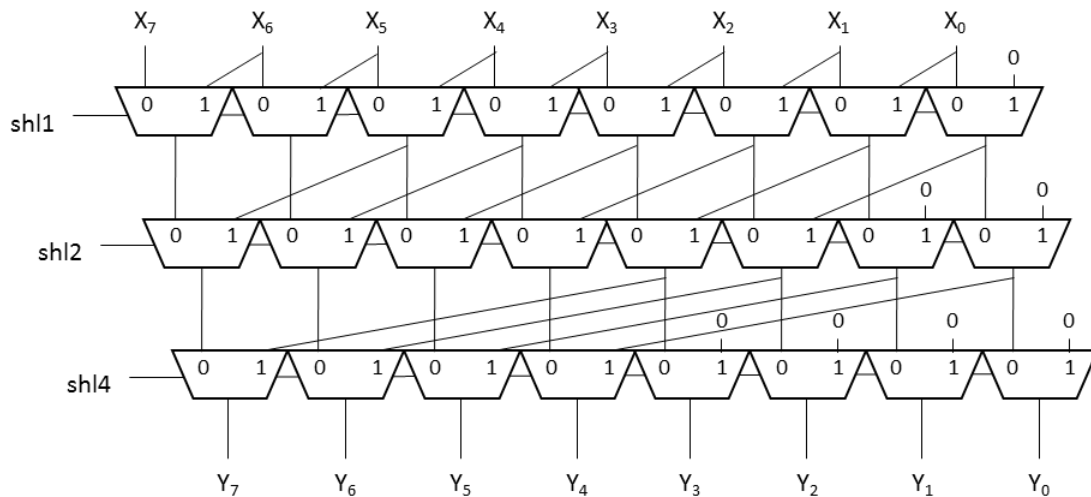


Figure 3

The input and output signals are illustrated in Figure 4.

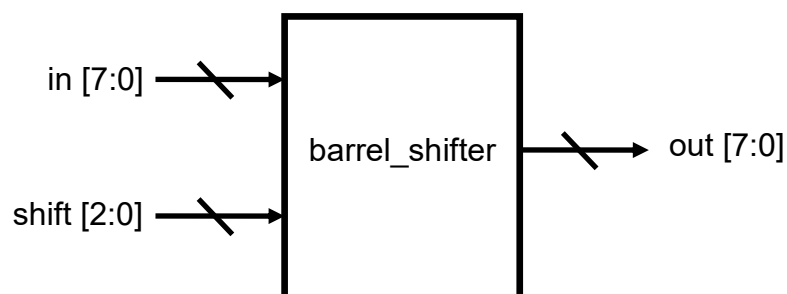


Figure 4

(1) (20%)

Modify the “barrel\_shifter\_gate.v” file. Use **gate level** description to design an 8-bit barrel shifter. Properly partition your design for clarity. Verify your design with “barrel\_gate\_test.v” by using the following command:

```
ncverilog barrel_gate_test.v barrel_shifter_gate.v +access+r
```

Show your waveform result in the report.

(2) (10%)

Design an 8-bit barrel-shifter with continuous assignment (use “**assign**”). Start with the “barrel\_shifter.v” file, which contains the module name and input/output ports. Verify your design with the given test bench, “barrel\_test.v”. Use the following command:

```
ncverilog barrel_test.v barrel_shifter.v +access+r
```

(3) (10%)

Illustrate the critical path of your design in the report and calculate the sum of delay. Specify 1ns delay for each Verilog primitive in (1). Try to modify the 2<sup>nd</sup> line in “barrel\_gate\_test.v”. Use different cycle time and report the correctness.

```
`define CYCLE 20.0
```

Verify the timing of your design with the following command:

```
ncverilog barrel_gate_test.v barrel_shifter_gate.v +access+r
```

### 3. Adder-Shifter Unit (20%)

Combine the previous two designs into an adder-shifter unit (Figure 5). The control signal “mode” is used to select the output from adder or barrel shifter. When mode = 1'b0, the out[7:0] is from barrel-shifter. When mode = 1'b1, out[7:0] is from adder. Note the “shift” input signal of the barrel-shifter is connected to the input Y[2:0]. At barrel-shifter mode, the output signal, “carry”, should keep 1'b0.

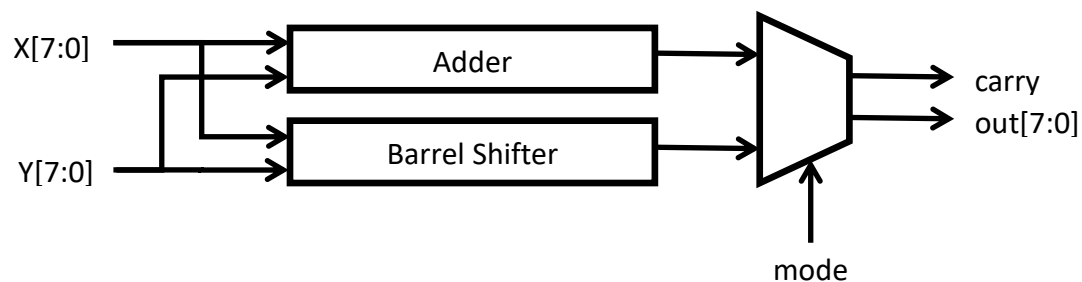


Figure 5

(1) (5%)

Instantiate the previously designed two transfer models (continuous assignment) in “asu.v” to implement the adder-shifter unit. Describe the mode multiplexer by using continuous assignment in “asu.v.” To run a simulation, **you need to put the related files in the same folder** and use the following command:

```
ncverilog asu_test.v asu.v adder.v barrel_shifter.v +access+r
```

(2) (5%)

Specify 2.5ns delay on the mode multiplexer in “asu.v” and save the file as “asu\_gate.v”. Use the gate-level design with specified delays in 1-(3) and 2-(3) to run the simulation again. Calculate the sum of delay on the critical path and verify the timing of your design by this command:

```
ncverilog asu_gate_test.v asu_gate.v adder_gate.v barrel_shifter_gate.v  
+access+r
```

Show your waveform result in the report.

(3) (5%)

Based on the result of the previous problems, the critical path may be on the adder or the barrel-shifter, followed by the mode multiplexer. Try to optimize the slower part with different structure (e.g. Carry Look Ahead Adder) in “adder\_gate\_opt.v” or “barrel\_shifter\_gate\_opt.v”. Calculate the sum of the delay on the critical path of the optimized design. Verify your result simulation and show your waveform result in the report.

```
ncverilog asu_gate_test.v asu_gate.v adder_gate_opt.v barrel_shifter_gate  
_opt.v +access+r
```

You need to describe how you optimize your design in the report.

(4) (5%)

Describe how to calculate unsigned multiplication with the adder-shifter unit.

You can assume there are other registers for storing temporary value.

#### **Submission requirement:**

1. All the files need to be compressed as a single **ZIP file** and **uploaded to Ceiba**.

#### **Example of filename**

DSD\_HW1\_b04901032.zip

Your submitted file should include the following files:

DSD\_HW1\_b04901032/

1-CR\_Adder/ adder.v adder\_gate.v

2-barrel\_shifter/ barrel\_shifter.v barrel\_shifter\_gate.v

3-ASU/ asu.v asu\_gate.v adder\_gate\_opt.v barrel\_shifter\_gate\_opt.v

report\_HW1\_b04901032.pdf

Note that you have to replace b04901032 with your student ID number.

2. **Deadline: 2021/03/18 23:59**
3. **The homework will be graded ONLY IF the filename of your submission is correct!**